

B

2

B.I

Q4)

$$HA_1 = L/2 + x \quad HA_2 = L/2 - x$$

$$g_1 = \rho \frac{HA_1}{S} = \rho \left(\frac{L}{2} + x \right) \quad g_2 = \rho \frac{HA_2}{S} = \rho \left(\frac{L}{2} - x \right)$$

$$\frac{g_2}{g_1} = \frac{\frac{L}{2} - x}{\frac{L}{2} + x} = \begin{cases} 1 & \text{pour } x = 0 \\ 0 & \text{pour } x = L/2 \\ \infty & \text{pour } x = -L/2 \end{cases}$$

B.II


Q5)

$$V_i + (\eta_1 // \eta_2) I_i = U$$

peute $-\frac{1}{g_1} - \frac{1}{g_2}$

$$g_{1/2} = g_0 \left(\frac{1 \pm x}{L} \right)$$

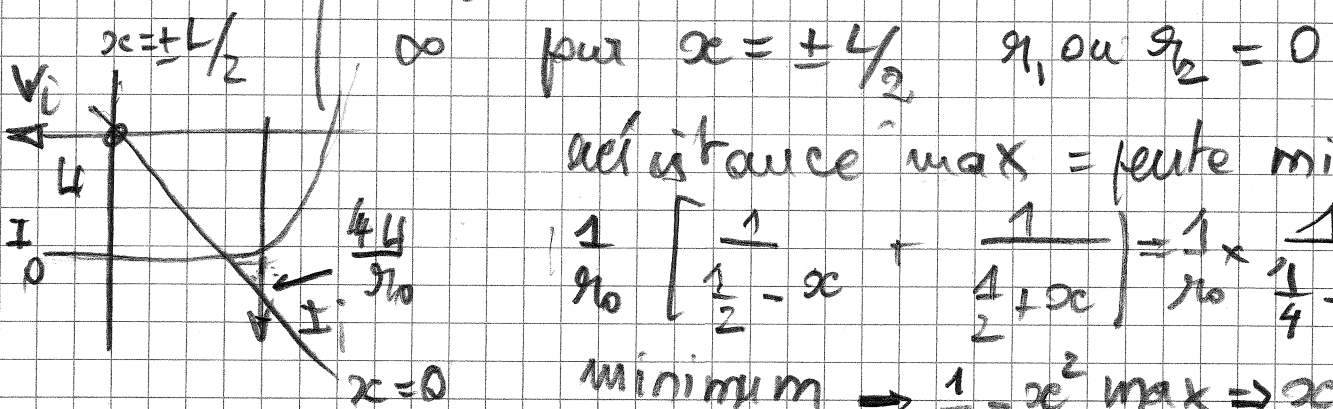peute = $\begin{cases} -\frac{4}{g_0} & \text{pour } x = 0 \\ \infty & \text{pour } x = \pm L/2 \end{cases} \quad (g_0/2) // (g_0/2)$



celle distance max = peute min

$$\frac{1}{g_0} \left[\frac{1}{L/2 - x} + \frac{1}{L/2 + x} \right] = \frac{1}{g_0} \times \frac{1}{\frac{1}{4} - x^2}$$

minimum $\rightarrow \frac{1}{4} - x^2$ max $\Rightarrow x = 0$

cas le plus exigeant $x = 0$

condition de plausation: $\frac{4U}{g_0} > I_0 \quad U > \frac{\eta_0 I_0}{4}$

Q6)

diviseur de courant

$$I_1 g_1 = I_2 g_2$$

$$\frac{I_2}{I_1} = \frac{g_1}{g_2} = \frac{L/2 + x}{L/2 - x} = \frac{1 + 2x/L}{1 - 2x/L}$$

$$I_1 = I_0 \frac{g_2}{g_1 + g_2} = I_0 \frac{HA_2}{A_1 A_2} = I_0 \left(\frac{1 - x}{L} \right)$$

$$I_2 = I_0 \frac{g_1}{g_1 + g_2} = I_0 \frac{HA_1}{A_1 A_2} = I_0 \left(\frac{1 + x}{L} \right)$$

$$\Rightarrow \Delta I = I_1 - I_2 = -2 I_0 \frac{x}{L} \quad \frac{\Delta I}{I_1} = -2 \frac{x}{L}$$